



# How electricity flows around a circuit

KS4 PHYSICS

Ages 11-14 ⌚ 3 min read

## What is a circuit?

A **circuit** is a closed loop that electricity travels around. It needs three main things to work: a **power source** (like a battery), **wires** to carry the electricity, and **components** (like light bulbs or motors) that use the electricity. If any part of the loop is broken, electricity cannot flow.

Think of it like a water slide at a swimming pool. Water flows down the slide, splashes into the pool, gets pumped back up, and slides down again. It keeps going round and round in a loop.

## How does electricity start flowing?

Inside a **battery**, chemical reactions create an **electric charge**. This charge builds up pressure, just like air pressure in a pump. The battery has two ends called **terminals**: the **positive terminal** (marked +) and the **negative terminal** (marked -). This difference in charge creates a force that pushes electricity out of the positive terminal through the circuit.

## Following the flow

Electricity flows from the positive terminal of the battery through the wires and components, and then back to the negative terminal. As it travels, it passes through **resistors** and other parts that slow it down and use its energy. This energy is what lights up a bulb or powers a motor.

Think of it like a postman delivering letters. The letter starts at the post office (battery), travels along streets (wires), gets delivered to houses (components), and eventually returns to the sorting office.

## Why does the loop matter?

The circuit must be a complete loop for electricity to flow. Even a tiny gap or **break** will stop everything. That's why a **switch** works—flipping it on or off opens or closes the loop. When you switch off a light, you're breaking the circuit.

## Speed and strength

Electricity doesn't actually travel very fast—about **one-third the speed of light**. But it feels instant to us because circuits are short. The amount of electricity flowing is called **current**, measured in **amps**. **Voltage** is the force pushing the electricity around, like water pressure in a pipe.

Think of voltage like the steepness of a hill and current like the amount of water flowing down it.