



---

# How Electricity Flows Through Circuits

KS3 Ages 11-14 ⌚ 3 min read

---

## What Is a Circuit?

A **circuit** is a closed loop that electricity travels around. It starts at the **power source** (like a battery), flows through **conductors** (usually wires), and powers devices like bulbs or motors before returning to the power source. Without a complete loop, electricity cannot flow.

Think of it like a train track. The train (electricity) needs a complete circular route to travel around. If the track is broken anywhere, the train stops and cannot complete its journey.

## How Does Electricity Flow?

Electricity flows from the **positive terminal** of a power source through a circuit to the **negative terminal**. This movement of **electrons** (tiny charged particles) creates electrical current. The electrons move very quickly, almost at the speed of light, even though each individual electron moves quite slowly through the wire.

**Conductors** like copper wire allow electrons to move easily because their atoms release electrons freely. **Insulators** like plastic or rubber prevent electricity flowing through them, which is why they wrap around wires to keep us safe.

## Open and Closed Circuits

A **closed circuit** has a complete, unbroken path, so electricity flows and devices work. An **open circuit** has a break in the path, so electricity stops flowing and devices turn off. A **switch** controls whether a circuit is open or closed by breaking or completing the path.

Think of it like a water pipe. When the tap is turned on (closed circuit), water flows. When you turn it off (open circuit), the water stops because the path is blocked.

## Resistance and Safety

**Resistance** is the opposition to electricity flowing through a material. Some materials resist electricity more than others. **Light bulbs** create resistance that slows down electrons, causing them to release energy as heat and light.

Too much current flowing through a circuit can be dangerous and cause fires. **Fuses** and **circuit breakers** protect buildings by breaking the circuit automatically if current becomes too high. This stops electricity flowing before damage or injury can happen.

Think of it like a crowd in a doorway. Too many people trying to squeeze through creates a dangerous jam, so security guards stop the flow to keep everyone safe.